

CIRCUITS

David Kauchak
CS 51 – Spring 2026

Admin



Assignment 3

Check autograder results after submitting assignment

Examples



The Logisim circuit examples can be found at:

<http://www.cs.pomona.edu/classes/cs51/circuits/>

Inside a CPU



Gates



Quick recap



$$\begin{array}{r} 01010 \\ + 01111 \\ \hline \end{array}$$


Quick recap




$$\begin{array}{r} 1\ 1\ 1\ 0 \\ 01010 \\ + 01111 \\ \hline 11001 \end{array}$$

A component
 
$$\begin{array}{r} \textcolor{blue}{1} \textcolor{blue}{1} \textcolor{red}{1} \textcolor{blue}{0} \\ 01\textcolor{orange}{0}10 \\ + 01\textcolor{green}{1}11 \\ \hline \textcolor{blue}{1} \textcolor{blue}{1} \textcolor{blue}{0} \textcolor{blue}{0} \textcolor{blue}{1} \end{array}$$




Adding with components

 


Adding with components
 
$$\begin{array}{r} 01010 \\ + 01111 \\ \hline \end{array}$$




Adding with components
 
$$\begin{array}{r} 0 \\ 01010 \\ + 01111 \\ \hline 1 \end{array}$$




Adding with components
 
$$\begin{array}{r} 10 \\ 01010 \\ + 01111 \\ \hline 01 \end{array}$$




Adding with components
 
$$\begin{array}{r} 110 \\ 01010 \\ + 01111 \\ \hline 001 \end{array}$$




Adding with components
 
$$\begin{array}{r} 1110 \\ 01010 \\ + 01111 \\ \hline 11001 \end{array}$$




Implementing the component

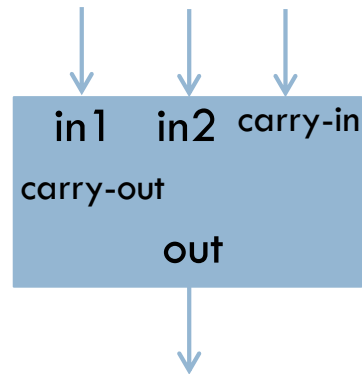

What goes on inside the component?


Implementing the component

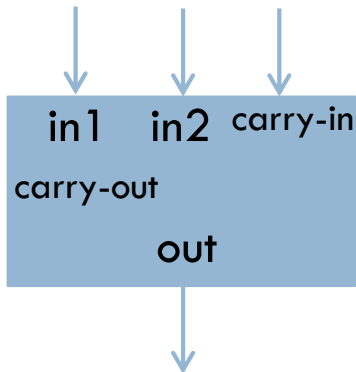

in1	in2	carry-in	out	carry-out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

What are the outputs?

Implementing the component

 

in1	in2	carry-in	out	carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Gates and Boolean logic

NOT ($\neg$) 

AND ($\wedge$) 

OR ($\vee$) 

XOR ($\oplus$) 

NAND ($\bar{\wedge}$) 



NOR ($\bar{\vee}$) 

X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

Gates have inputs and outputs
values are 0 or 1


They are **hardware** components!

Gates as hardware

  


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Utilizing gates

 

X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

$\neg$
not

 

$\wedge$
and



$\vee$
or



$\oplus$
xor




$\bar{\wedge}$
nand



$\bar{\vee}$
nor




Utilizing gates

 


X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

$\neg$
not

 

$\wedge$
and

 


$\vee$
or



$\oplus$
xor




$\bar{\wedge}$
nand

 

$\bar{\vee}$
nor




Utilizing gates

 


X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

$\neg$
not

 

$\wedge$
and

 


$\vee$
or



$\oplus$
xor




$\bar{\wedge}$
nand

 

$\bar{\vee}$
nor




Utilizing gates

 


X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

When is this circuit 1?

$\neg$
not

 

$\wedge$
and

 

$\vee$
or



$\oplus$
xor




$\bar{\wedge}$
nand



$\bar{\vee}$
nor



Utilizing gates

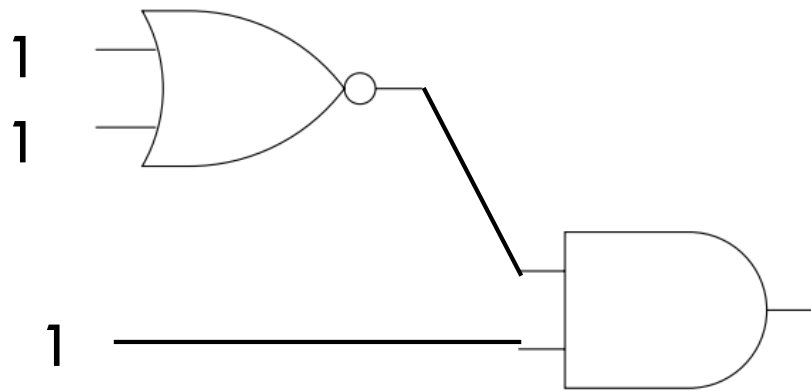

X	Y	Z	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


Designing more interesting circuits

X	Y	Z	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


Design a circuit for this

X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

$\neg$
not

 

$\wedge$
and

 

$\vee$
or



$\oplus$
xor



$\bar{\wedge}$
nand




$\bar{\vee}$
nor



Designing more interesting circuits

X	Y	Z	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 


Designing more interesting circuits

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


Design a circuit for this

X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0

$\neg$
not

 

$\wedge$
and

 

$\vee$
or



$\oplus$
xor



$\bar{\wedge}$
nand



$\bar{\vee}$
nor



Truth table to Boolean expression


What approaches have we seen for developing a Boolean expression from a truth table?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Truth table to Boolean expression

What approaches have we seen for developing a Boolean expression from a truth table?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

minterm expansion (DNF
– OR of ANDs)

maxterm expansion (CNF
– AND of ORs)


K-Maps (OR of ANDs)

Minterm expansion


All these should be 1 and everything else 0

X	Y	Z	OUT	Minterm
0	0	0	1	$\neg X \wedge \neg Y \wedge \neg Z$
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	1	$X \wedge \neg Y \wedge \neg Z$
1	0	1	0	
1	1	0	1	$X \wedge Y \wedge \neg Z$
1	1	1	0	

Minterm expansion

 


Minterm expansion

 

When will this AND-gate be 1?


Minterm expansion

 

Only when $X=0, Y=0, Z=0$


X	Y	Z	OUT	Minterm
0	0	0	1	$\neg X \wedge \neg Y \wedge \neg Z$

Minterm expansion

 

When will this AND-gate be 1?

Minterm expansion

 


Only when $\text{in1}=1, \text{in2}=0, \text{in3}=0$

X	Y	Z	OUT	Minterm
1	0	0	1	$X \wedge \neg Y \wedge \neg Z$

Minterm expansion


X	Y	Z	OUT	Minterm
0	0	0	1	$\neg X \wedge \neg Y \wedge \neg Z$
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	1	$X \wedge \neg Y \wedge \neg Z$
1	0	1	0	
1	1	0	1	$X \wedge Y \wedge \neg Z$
1	1	1	0	

 

Make a conjunction for each minterm

Minterm expansion


X	Y	Z	OUT	Minterm
0	0	0	1	$\neg X \wedge \neg Y \wedge \neg Z$
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	1	$X \wedge \neg Y \wedge \neg Z$
1	0	1	0	
1	1	0	1	$X \wedge Y \wedge \neg Z$
1	1	1	0	

 

How do we combine these?

Minterm expansion

X	Y	Z	OUT	Minterm
0	0	0	1	$\neg X \wedge \neg Y \wedge \neg Z$
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	1	$X \wedge \neg Y \wedge \neg Z$
1	0	1	0	
1	1	0	1	$X \wedge Y \wedge \neg Z$
1	1	1	0	

 

OR-gate: $(\neg X \wedge \neg Y \wedge \neg Z) \vee (X \wedge \neg Y \wedge \neg Z) \vee (X \wedge Y \wedge \neg Z)$

K-maps

Can you use a K-map to come up with a Boolean expression for this table?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

K-maps

Can you use a K-map to come up with a Boolean expression for this table?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


		YZ			
		00	01	11	10
X	0	1	0	0	0
	1	1	0	0	1

What is the Boolean expression?

K-maps

Can you use a K-map to come up with a Boolean expression for this table?


X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

K-maps

Can you design a circuit?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$(\neg Y \wedge \neg Z) \vee (X \wedge \neg Z)$$

K-maps


Can you design a circuit?

X	Y	Z	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

Back to addition...

in1	in2	carry-in	carry-out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

A half-adder: no carry-in


A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

X	Y	$\neg X$	$X \wedge Y$	$X \vee Y$	$X \oplus Y$	$X \bar{\wedge} Y$	$X \bar{\vee} Y$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	1	0
1	1	0	1	1	0	0	0


Hint: solve each output bit independently

Design a circuit for this

$\neg$
not

 

$\wedge$
and

 

$\vee$
or



$\oplus$
xor



$\bar{\wedge}$
nand




$\bar{\vee}$
nor




A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


higher order bit of A+B


Implementing a full adder

 


Implementing a full adder

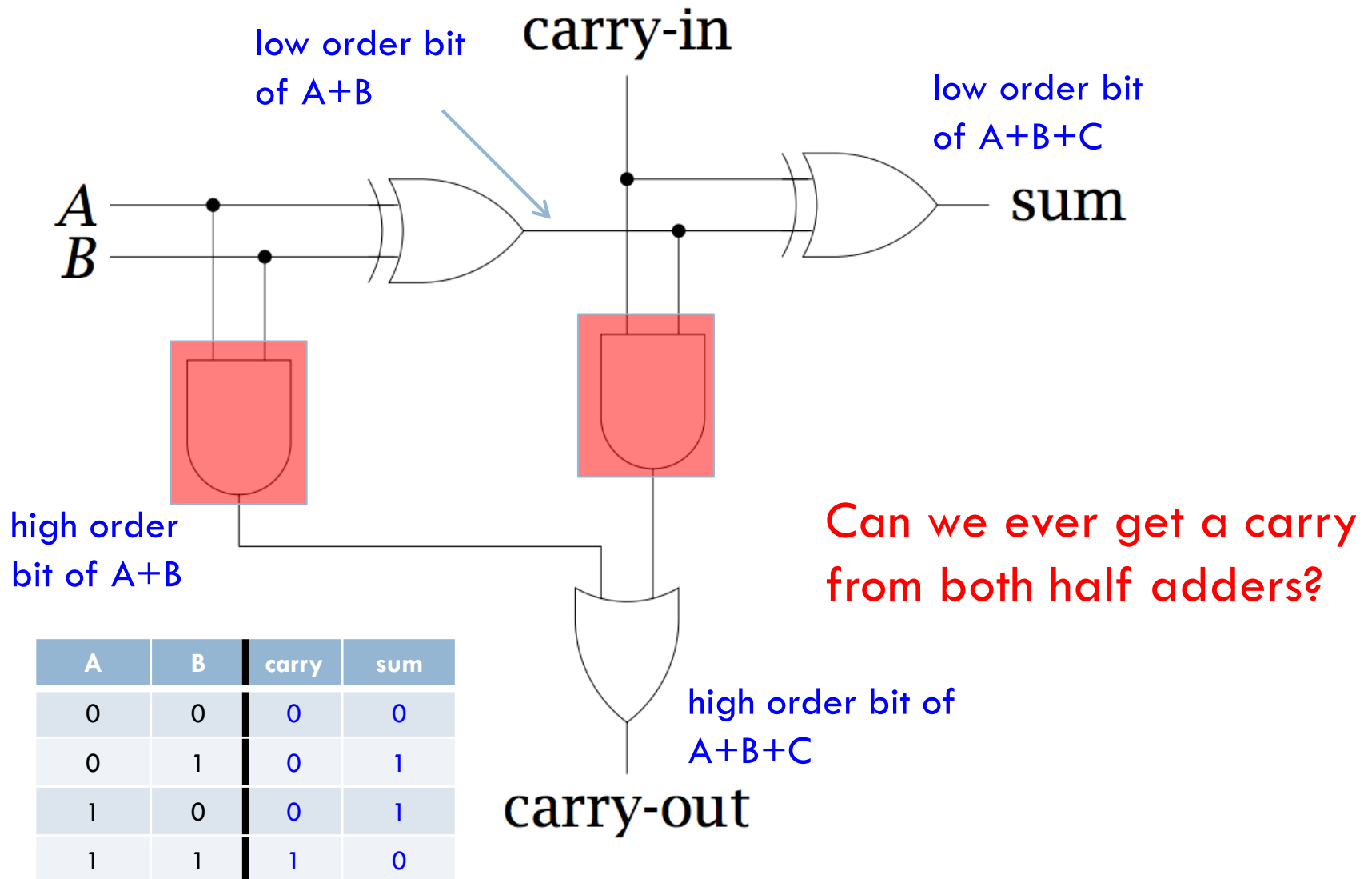

Implementing a full adder

 


Implementing the component

 

What goes on inside the component?

Implementing the component

 


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

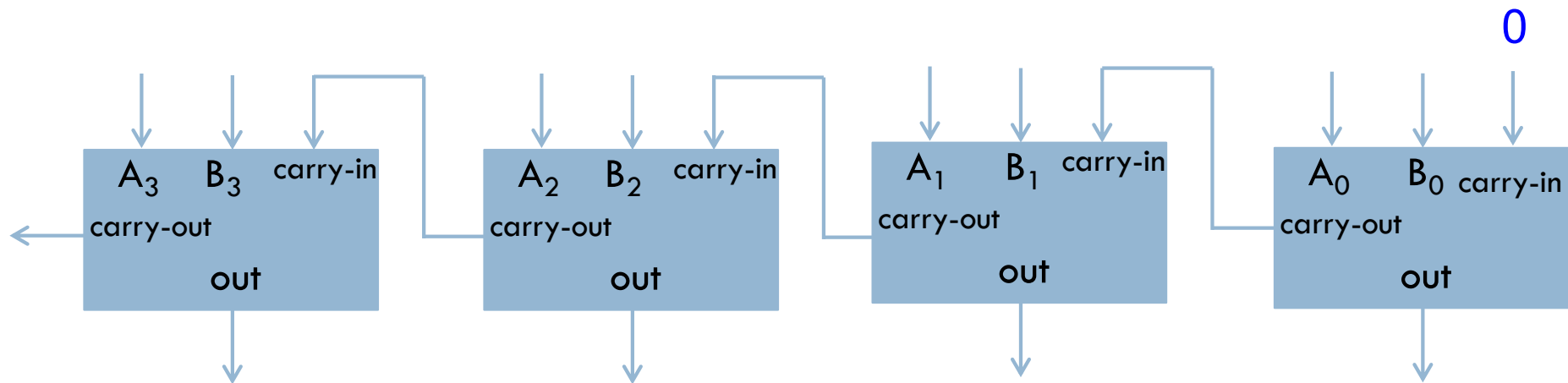

Any downsides (computationally) to ripple carry adder?

Look at ripple carry adder example




Many circuits

- ▣ half-adder
- ▣ full-adder (using half-adders)
- ▣ ripple-carry adder (using full-adders)

Simulator basics




Mystery circuit

 

d_1	d_0	out_0	out_1	out_3	out_3
0	0				
0	1				
1	0				
1	1				

What does this circuit do?


2-bit decoder

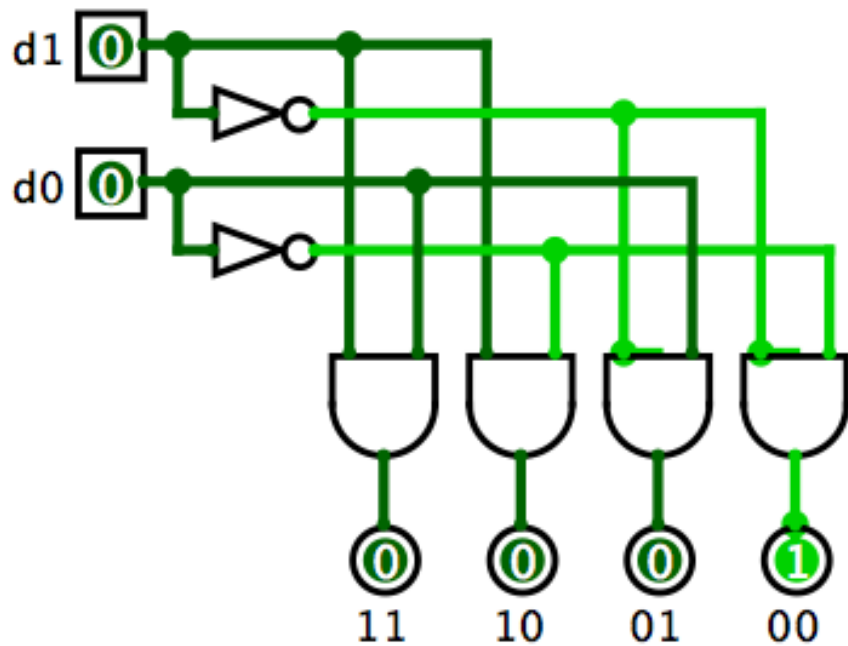

d_1	d_0	out ₀	out ₁	out ₂	out ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


Sends '1' along one of the output lines

2-bit decoder*

 

What does the extra input do?

2-bit decoder*

 

When 0, doesn't select any lines, when 1, functions normally

3-bit decoder



3 inputs

How many output lines?

3-bit decoder

3 inputs

8 output lines

Inputs			Outputs							
d_2	d_1	d_0	t_{000}	t_{001}	t_{010}	t_{011}	t_{100}	t_{101}	t_{110}	t_{111}
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

3-bit decoder

3 inputs



8 output lines

Inputs			Outputs							
d_2	d_1	d_0	t_{000}	t_{001}	t_{010}	t_{011}	t_{100}	t_{101}	t_{110}	t_{111}
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Could make from scratch


Better idea: reuse 2-bit decoders

3-bit decoder

  


Could we use two 2-bit decoders?

3-bit decoder

 

d2 gets sent to the enable of the two 2-bit decoders. One as normal and one negated.

3-bit decoder using 2-bit decoders

 

Look at decoders in simulator



Examples



The Logisim circuit examples can be found at:

<http://www.cs.pomona.edu/classes/cs51/circuits/>

You can download Logism Evolution at:

<https://github.com/logisim-evolution/logisim-evolution>